



# Sunrise 3 Hardware Reference Design Errata

---

Rev. 0.4

July 12, 2021

## Revision History

This section tracks the significant documentation changes that occur from release-to-release. The following table lists the technical content changes for each revision.

Revision	Date	Description
V 0.1	2020-11-12	Initial Draft for VAA ramp up rate issue and reset circuit
V0.2	2020-11-25	Add Design note for CNN power supply
V0.3	2021-01-28	Add Section 2.4 USB device hot plug support.
V0.4	2021-07-12	Add Section 2.5 EFUSE_VDD Connection

## Contents

Revision History.....	2
Figures.....	4
Tables.....	5
1 Scope.....	6
2 Schematic Design Note .....	6
2.1 DDR PHY power rail ramp up rate.....	6
2.2 Reset Circuit .....	8
2.3 CNN Power supply .....	8
2.4 USB Device mode Hot-plug Support.....	9
2.5 EFUSE_VDD Connection .....	11

## Figures

Figure 2-1 Sunrise 3 integrated ESD protection .....	6
Figure 2-2 DDR PHY VAA ramp up rate control circuit .....	7
Figure 2-3 External POR reset circuit.....	8
Figure 2-4 CNN Power supply transient voltage drop .....	9
Figure 2-5 VBUS Insertion Detection Solution.....	10
Figure 2-6 USB VBUS Controlled Power up for X3 .....	11
Figure 2-7 EFUSE VDD Connection.....	11
Figure 2-8 EFUSE_VDD on/off Sequence.....	12

## Tables

Table 1-1 applicable reference design revision .....	6
Table 2-1 Sunrise 3 power ramp up rate requirements .....	7
Table 2-2 passive components value recommendation .....	7
Table 2-3 Reference DCDC/PMIC transient load response requirement.....	9
Table 2-4 Suggested Bulk Capacitor Part Number .....	9
Table 2-5 CNN0/1 power supply .....	9

## 1 Scope

This document describes the potential problems found during the verification of the Sunrise 3 DVB. The documents is applicable to the following Sunrise 3 DVB schematic and PCB layout revision.

Table 1-1 applicable reference design revision

Design	Filename
<b>Schematic</b>	SC-2510-2-2a-dv-sm-01a_20200826a
	SC-2510-3-2a-dv-sm-01b_20200826a
	SC-2510-6-2A-DV-SM-01C_20200907
<b>PCB</b>	LO-2510-2-2A-DV-SM-01A_11221500
	LO-2510-3-2A-DV-SM-01B_ddr4_202001201530
	LO-2510-6-2A-DV-SM-01C_20200828

## 2 Schematic Design Note

### 2.1 DDR PHY power rail ramp up rate

#### Issue description:

Some of the Power rails of Sunrise 3 integrate a typical ESD protection circuit depicted by the following figure.

When VDD ramp up too fast (ESD transient), the RC delay circuit will keep Vrc low and Vg high, then Mesd will be opened to sink the ESD transient to VSS.

However, if normal power up event has too fast ramp up rate, it will mis-trigger the Mesd and has the very small potential to damage the Mesd after numerous power-up events.

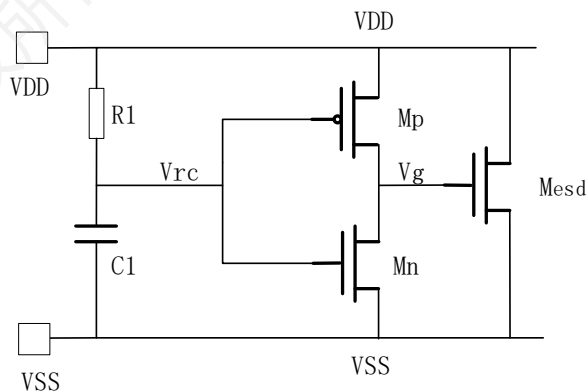


Figure 2-1 Sunrise 3 integrated ESD protection

The following table summarizes the requirements on the ramp up rate of Sunrise 3 's power rails.

Table 2-1 Sunrise 3 power ramp up rate requirements

Power rail	VDDQ_DDR	VP_MIP1	VDD_USB	EFUSE_VDD	ARMPLL_VDDPST	Others
	VDDQLP_DDR	VPH_MIP1	VP_USB		ARMPLL_VDDHV	
	VAA		VPH_USB		ARMPLL_VDDREF	
Ramp up rate	<5mV/us	<100mV/us	<100mV/us	<60mV/us	No requirement	<18mV/us

Regarding the Sunrise 3 reference design, the failed power rail is VAA and PVT\_VDDA\_TAVDD. The actual measured ramp up rate is around 25mV/us.

### Workaround:

There are two options to eliminate the potential risk.

- One option is to use a discrete LDO power supply which has < 5mV/us ramp up rate.
- The 2<sup>nd</sup> option is to use the following soft start circuit between the LDO output and VAA.

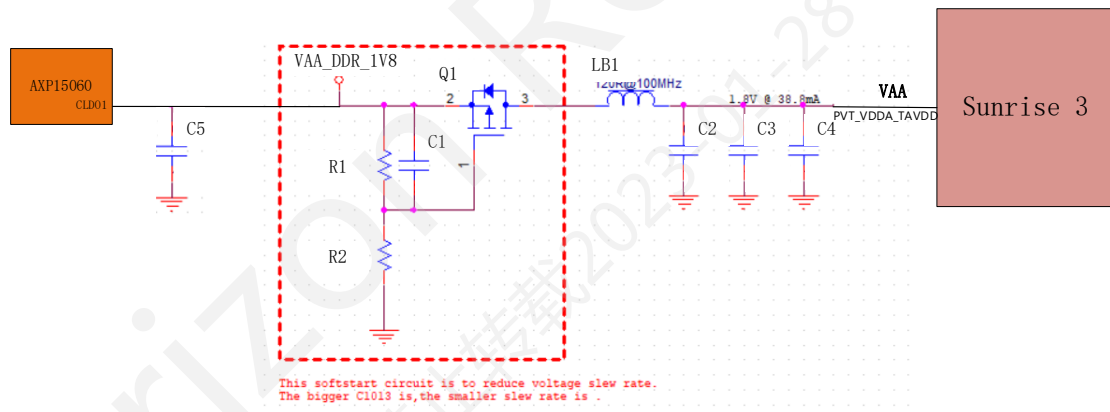


Figure 2-2 DDR PHY VAA ramp up rate control circuit

The following table describes the recommended value for passive components.

Table 2-2 passive components value recommendation

Ref.	Value	Vendor	Part number	Notes
<b>C1</b>	2.2uF	-	-	3
<b>C2</b>	10uF	-	-	-
<b>C3</b>	1uF	-	-	-
<b>C4</b>	0.1uF	-	-	-
<b>C5</b>	4.7uF	-	-	-
<b>R1</b>	100K Ohm	-	-	-

<b>R2</b>	10K Ohm	-	-	-
<b>Q1</b>	-	NEXPERIA	PMV160UP	1,2
<b>LB1</b>	120Ohm@100Mhz	-	-	-

**Notes:**

1. select Q1 with small  $R_{ds(on)}$  ( $< 200m\Omega$ ) and continuous  $I_d$  drain current  $> 200mA$
2. Make sure voltage feed into VAA still meets the ripple requirement ( $1.8V \pm 2.5\%$ )
3. Adjust the value of C1 to achieve  $< 5mV/\mu s$  ramp up rate.

## 2.2 Reset Circuit

Sunrise 3 needs external Power-On-Reset (POR) input through RSTN pin to reset the entire chip. The RSTN should be stable more than 10ms after all the power groups (1/2/3/4) achieve target value and 24MHz main clock is active and stable.

Figure 2-3 shows the recommended connection of external POR circuit.

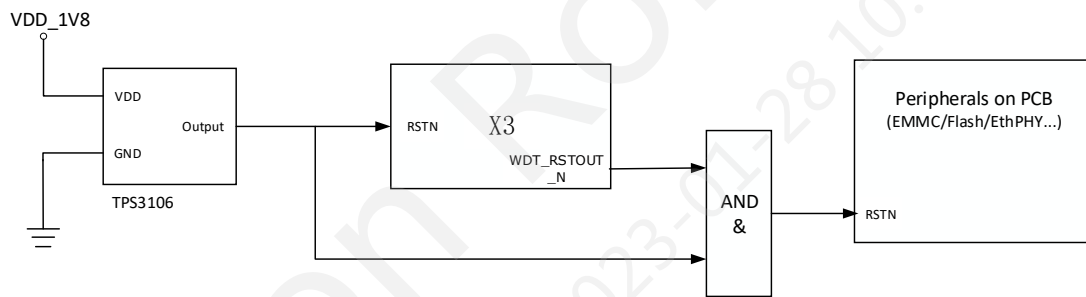


Figure 2-3 External POR reset circuit

WDT\_RSTOUT\_N is an active-low reset output signal and generated by X3 watchdog timeout event, it is used to reset peripherals on the board, EMMC, Flash, Ethernet PHY, etc.

**Note:** WDT\_RSTOUT\_N signal needs to be sent to peripherals on the board especially memory devices (EMMC and Flash) and can't be sent back to X3's RSTN input signal via PCB trace.

## 2.3 CNN Power supply

**Issue description:**

Because Sunrise3's CNN behavior causes much higher  $di/dt$  (current variation over time) than other core power supply, the power supply to CNN core needs to have better transient load response performance. Otherwise, transient voltage drop will occur on VRM's output. Please check the following figure for this phenomenon.



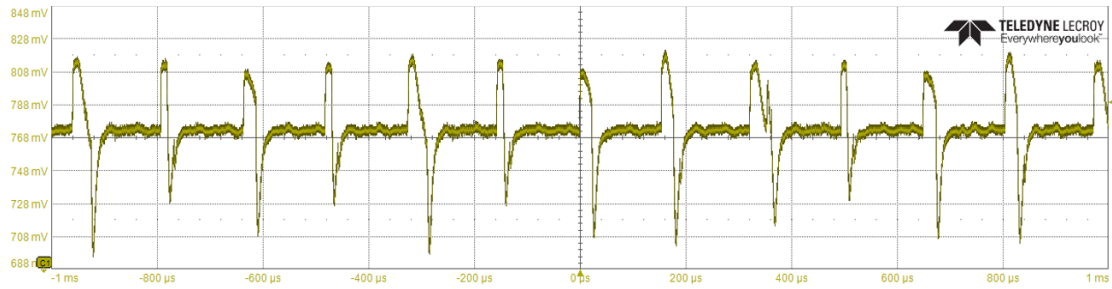


Figure 2-4 CNN Power supply transient voltage drop

### Workaround:

To mitigate the potential problem caused by the voltage drop, there are 2 ways to improve the situation.

- ◆ First way is to choose a DCDC/PMIC with better transient load response performance, the following table depicts a reference requirement for DCDC/PMIC transient load response.

Table 2-3 Reference DCDC/PMIC transient load response requirement

Transient load regulation	Undershoot	Overshoot
<b>Under typical Cout</b> <b>Iload (di/dt) = 2A/us</b>	Vout – 25mV	Vout + 25mV

- ◆ 2<sup>nd</sup> way is to increase Cout to BIGGER value if the PCB space could accommodate the extra component. The following table gives some reference part number which could be used. Customer could choose their own part number with enough capacitance and small ESR.

Table 2-4 Suggested Bulk Capacitor Part Number

Vendor	Part Number	Value	ESR
<b>Panasonic</b>	EEFSX0D331XE	330uF	6 mΩ max
<b>Panasonic</b>	EEFSX0D471ER	470uF	9 mΩ max

**NOTE:** Balance the DCDC/PMIC selection and Bulk capacitor selection to achieve the result depicted by following table. Be noted that the measurement should be done under customer typical scenario with BPU in maximum loading.

Table 2-5 CNN0/1 power supply

Power rail	Typical voltage	V peak to peak
VDD_CNN0/1	0.82V	< 82mV (+/-5%)

## 2.4 USB Device mode Hot-plug Support

### Issue description:

When Sunrise3 acts as USB device, extra consideration should be taken to support the Hot-plug feature.

USB\_VBUS pin is not functional available at the package ball. The  $30K\ \Omega$  pull up resistor is no longer needed, and the VBUS detection is also not available through USB\_VBUS pin.

### Workaround:

**Solution A:** use a separate GPIO to detect the VBUS insertion. Please refer to the Figure 2-5 for the detail connection. Dedicated software thread is needed for GPIO status polling.

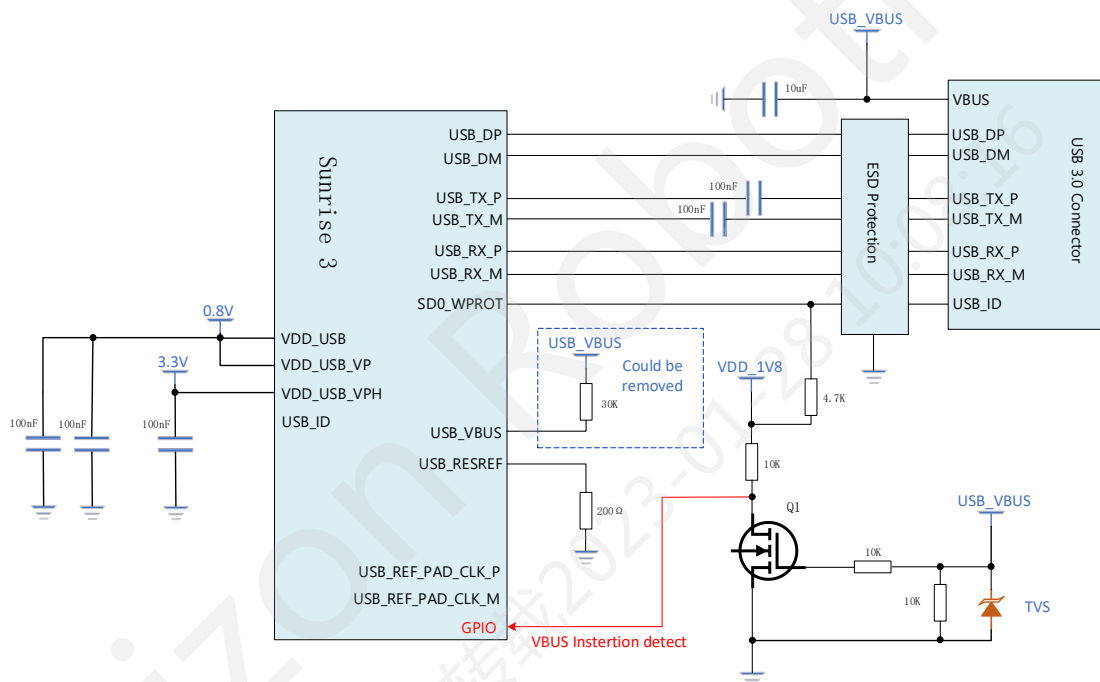


Figure 2-5 VBUS Insertion Detection Solution

**Solution B:** Use USB\_VBUS as enable signal to the X3's PMIC output. X3 will not power up without USB\_VBUS inserted. This is common in Smart USB Camera scenario. Please refer to the Figure 2-6 for this solution.

 


Figure 2-6 USB VBUS Controlled Power up for X3

## 2.5 EFUSE\_VDD Connection

### Issue description:

EFUSE\_VDD is default powered up by 1.8V LDO output. EFUSE\_VDD needs only to be powered up while burning X3 EFUSE, and it should be connected to ground or left floating in all other situation except burning EFUSE. Otherwise, there is very small chance that the EFUSE content is mistakenly changed.

### Workaround:

Connect EFUSE\_VDD to the test pad instead of 1.8V.

EFUSE\_VDD will be floating in customer normal scenario. When customer needs to change the content of EFUSE in production line, use production jig to short the EFUSE\_VDD to 1.8V.

The short behavior needs to be controlled by SW to make sure that the EFUSE\_VDD on/off sequence describe in Figure 2-8 is fulfilled.

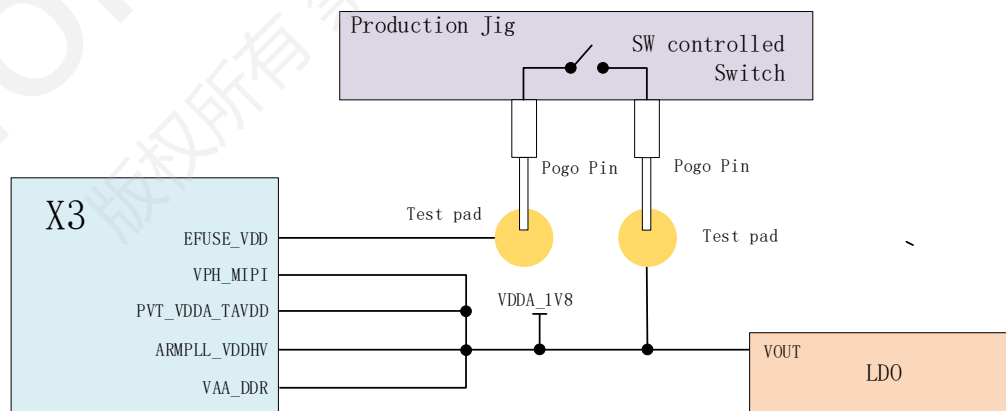


Figure 2-7 EFUSE VDD Connection

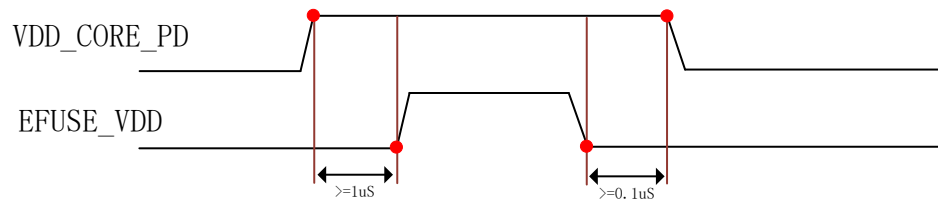


Figure 2-8 EFUSE\_VDD on/off Sequence